


Vypracovanie PC_6

Alexander Bekeč, 221096

Link to depository: <https://github.com/alexander-bekec/Digital-electronics-1>

1. Preparation task

Timing diagram

 

2. Display driver

Multiplexer proces design

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dp_o <= dp_i(3);
            dig_o <= "0111";

        when "10" =>
            s_hex <= data2_i;
            dp_o <= dp_i(2);
            dig_o <= "1011";

        when "01" =>
            s_hex <= data1_i;
            dp_o <= dp_i(1);
            dig_o <= "1101";
```

```

        when others =>
            s_hex <= data0_i;
            dp_o  <= dp_i(0);
            dig_o <= "1110";
        end case;
    end process p_mux;

```

Testbench

```

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;

-----
-- Architecture body for testbench
-----
architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time    := 10 ns;

    --Local signals
    signal s_clk_100MHz : std_logic;
    signal s_reset : std_logic;
    signal s_data0_i : std_logic_vector(4-1 downto 0);
    signal s_data1_i : std_logic_vector(4-1 downto 0);
    signal s_data2_i : std_logic_vector(4-1 downto 0);
    signal s_data3_i : std_logic_vector(4-1 downto 0);
    signal s_dp_i : std_logic_vector(4-1 downto 0);

    signal s_dp_o : std_logic;
    signal s_dig_o : std_logic_vector(4-1 downto 0);
    signal s_seg_o : std_logic_vector(7-1 downto 0);

begin
    -- Connecting testbench signals with driver_7seg_4digits entity
    -- (Unit Under Test)
    uut_display_driver : entity work.driver_7seg_4digits
        port map(
            reset => s_reset,
            clk => s_clk_100MHz,
            data0_i => s_data0_i,
            data1_i => s_data1_i,

```

```

        data2_i => s_data2_i,
        data3_i => s_data3_i,
        dp_i => s_dp_i,
        seg_o => s_seg_o,
        dig_o => s_dig_o,
        dp_o => s_dp_o
    );

-----
-- Clock generation process
-----

p_clk_gen : process
begin
    while now < 750 ns loop          -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Reset generation process
-----

p_reset_gen : process
begin
    s_reset <= '1';
    wait for 12 ns;

    s_reset <= '0';
    wait for 120 ns;

    s_reset <= '1';
    wait for 12 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_data0_i <= "0010";
    s_data1_i <= "0100";
    s_data2_i <= "0001";
    s_data3_i <= "0011";
    s_dp_i <= "0111";
    wait for 600 ns;

    s_data0_i <= "0111";

```

```

        s_data1_i <= "1000";
        s_data2_i <= "0110";
        s_data3_i <= "0101";
        s_dp_i <= "1011";
        report "Stimulus process finished" severity note;
        wait;
    end process p_stimulus;

end architecture testbench;

```

Simulation Waveform



g_MAX of the clock_enable was changed to 4 instead of 400000.

Top

```

architecture Behavioral of top is
    -- No internal signals
begin

    -----
    -- Instance (copy) of driver_7seg_4digits entity
    driver_seg_4 : entity work.driver_7seg_4digits
        port map(
            clk          => CLK100MHZ,
            reset        => BTNC,

            data0_i(3) => SW(3),
            data0_i(2) => SW(2),
            data0_i(1) => SW(1),
            data0_i(0) => SW(0),

            data1_i(3) => SW(7),
            data1_i(2) => SW(6),
            data1_i(1) => SW(5),
            data1_i(0) => SW(4),

            data2_i(3) => SW(11),
            data2_i(2) => SW(10),
            data2_i(1) => SW(9),
            data2_i(0) => SW(8),

```

```

data3_i(3) => SW(15),
data3_i(2) => SW(14),
data3_i(1) => SW(13),
data3_i(0) => SW(12),

dp_i => "0111",

seg_o(6) => CA,
seg_o(5) => CB,
seg_o(4) => CC,
seg_o(3) => CD,
seg_o(2) => CE,
seg_o(1) => CF,
seg_o(0) => CG,

dig_o(4 downto 0) => AN(4 downto 0)
);

-- Disconnect the top four digits of the 7-segment display
AN(7 downto 4) <= b"1111";

end architecture Behavioral;

```

3. Eight-digit driver

