

Vypracovanie PC_2

Alexander Bekeč, 221096

Link to depository: <https://github.com/alexander-bekec/Digital-electronics-1>

1. Preparation task

| Dec. equivalent | B[1:0] | A[1:0] | B is greater than A | B equals A | B is less than A |
|-----------------|--------|--------|---------------------|------------|------------------|
| 0 | 0 0 | 0 0 | 0 | 1 | 0 |
| 1 | 0 0 | 0 1 | 0 | 0 | 1 |
| 2 | 0 0 | 1 0 | 0 | 0 | 1 |
| 3 | 0 0 | 1 1 | 0 | 0 | 1 |
| 4 | 0 1 | 0 0 | 1 | 0 | 0 |
| 5 | 0 1 | 0 1 | 0 | 1 | 0 |
| 6 | 0 1 | 1 0 | 0 | 0 | 1 |
| 7 | 0 1 | 1 1 | 0 | 0 | 1 |
| 8 | 1 0 | 0 0 | 1 | 0 | 0 |
| 9 | 1 0 | 0 1 | 1 | 0 | 0 |
| 10 | 1 0 | 1 0 | 0 | 1 | 0 |
| 11 | 1 0 | 1 1 | 0 | 0 | 1 |
| 12 | 1 1 | 0 0 | 1 | 0 | 0 |
| 13 | 1 1 | 0 1 | 1 | 0 | 0 |
| 14 | 1 1 | 1 0 | 1 | 0 | 0 |
| 15 | 1 1 | 1 1 | 0 | 1 | 0 |

$$equals_{SOP} = (\overline{B_1} \cdot \overline{B_0} \cdot \overline{A_1} \cdot \overline{A_0}) + (\overline{B_1} \cdot B_0 \cdot \overline{A_1} \cdot A_0) + (B_1 \cdot \overline{B_0} \cdot A_1 \cdot \overline{A_0}) + (B_1 \cdot B_0 \cdot A_1 \cdot A_0)$$

$$less_{POS} = (B_1 + B_0 + A_1 + A_0) \cdot (B_1 + \overline{B_0} + A_1 + A_0) \cdot (B_1 + \overline{B_0} + A_1 + \overline{A_0}) \cdot (\overline{B_1} + B_0 + A_1 + A_0) \cdot (\overline{B_1} + B_0 + A_1 + \overline{A_0}) \cdot (\overline{B_1} + B_0 + \overline{A_1} + A_0) \cdot (\overline{B_1} + \overline{B_0} + A_1 + A_0) \cdot (\overline{B_1} + \overline{B_0} + A_1 + \overline{A_0}) \cdot (\overline{B_1} + \overline{B_0} + \overline{A_1} + A_0) \cdot (\overline{B_1} + \overline{B_0} + \overline{A_1} + \overline{A_0})$$

2. 2-bit comparator

| B equals A | | | | | A_1 | |
|------------|-------|----|----|-------|-------|----|
| | | | | A_0 | | |
| | | | 00 | 01 | 11 | 10 |
| B_1 | B_0 | 00 | 1 | 0 | 0 | 0 |
| | | 01 | 0 | 1 | 0 | 0 |
| | | 11 | 0 | 0 | 1 | 0 |
| | | 10 | 0 | 0 | 0 | 1 |


| B greater than A | | | | | A_1 | |
|------------------|-------|----|----|-------|-------|----|
| | | | | A_0 | | |
| | | | 00 | 01 | 11 | 10 |
| B_1 | B_0 | 00 | 0 | 0 | 0 | 0 |
| | | 01 | 1 | 0 | 0 | 0 |
| | | 11 | 1 | 1 | 0 | 1 |
| | | 10 | 1 | 1 | 0 | 0 |

$greater_{SoP_{min}} = (B_1 \cdot \overline{A_1}) + (B_0 \cdot \overline{A_1} \cdot \overline{A_0}) + (B_1 \cdot B_0 \cdot \overline{A_0})$

| | | | | | | |
|---------------|-------|----|----|-------|-------|----|
| B less than A | | | | | A_1 | |
| | | | | A_0 | | |
| | | | 00 | 01 | 11 | 10 |
| B_1 | B_0 | 00 | 0 | 1 | 1 | 1 |
| | | 01 | 0 | 0 | 1 | 1 |
| | | 11 | 0 | 0 | 0 | 0 |
| | | 10 | 0 | 0 | 1 | 0 |

$$less_{PoS_{min}} = (A_1 + A_0) \cdot (\overline{B_1} + \overline{B_0}) \cdot (\overline{B_1} + A_0) \cdot (\overline{B_1} + A_1) \cdot (\overline{B_0} + A_1)$$

<https://www.edaplayground.com/x/MyMd>

 

3. 4-bit comparator

<https://www.edaplayground.com/x/wYGV>

```
-- design.vhd
library IEEE;
use IEEE.std_logic_1164.all;

entity comparator_4bit is
  port(
    a_i      : in  std_logic_vector(4 - 1 downto 0);
    b_i      : in  std_logic_vector(4 - 1 downto 0);
```

```

        B_greater_A_o : out std_logic;
        B_equals_A_o  : out std_logic;
        B_less_A_o    : out std_logic
    );
end entity comparator_4bit;

architecture Behavioral of comparator_4bit is
begin
    B_less_A_o    <= '1' when (b_i < a_i) else '0';
    B_equals_A_o  <= '1' when (b_i = a_i) else '0';
    B_greater_A_o <= '1' when (b_i > a_i) else '0';
end architecture Behavioral;

```

```

-- testbench.vhd + error at 255
library IEEE;
use IEEE.std_logic_1164.all;

entity tb_comparator_4bit is

end entity tb_comparator_4bit;

architecture testbench of tb_comparator_4bit is

    signal s_a      : std_logic_vector(4 - 1 downto 0);
    signal s_b      : std_logic_vector(4 - 1 downto 0);
    signal s_B_greater_A : std_logic;
    signal s_B_equals_A  : std_logic;
    signal s_B_less_A    : std_logic;

begin
    uut_comparator_4bit : entity work.comparator_4bit
        port map(
            a_i      => s_a,
            b_i      => s_b,
            B_greater_A_o => s_B_greater_A,
            B_equals_A_o  => s_B_equals_A,
            B_less_A_o    => s_B_less_A
        );

    p_stimulus : process
    begin
        report "Stimulus process started" severity note;

        s_b <= "0000"; s_a <= "0000"; wait for 100 ns;
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '1') and (s_B_less_A =
'0'))
        report "Test failed for input combination: (0) 0000, 0000" severity error;

        s_b <= "0000"; s_a <= "1001"; wait for 100 ns;
        assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))

```

```
report "Test failed for input combination: (9) 0000, 1001" severity error;

s_b <= "0010"; s_a <= "1010"; wait for 100 ns;
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
report "Test failed for input combination: (42) 0010, 1010" severity
error;

s_b <= "0010"; s_a <= "1111"; wait for 100 ns;
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
report "Test failed for input combination: (47) 0010, 1111" severity
error;

s_b <= "0100"; s_a <= "0101"; wait for 100 ns;
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
report "Test failed for input combination: (69) 0100, 0101" severity
error;

s_b <= "0110"; s_a <= "0000"; wait for 100 ns;
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
report "Test failed for input combination: (96) 0110, 0000" severity
error;

s_b <= "0111"; s_a <= "1001"; wait for 100 ns;
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
report "Test failed for input combination: (121) 0111, 1001" severity
error;

s_b <= "1001"; s_a <= "0000"; wait for 100 ns;
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
report "Test failed for input combination: (144) 1001, 0000" severity
error;

s_b <= "1010"; s_a <= "1001"; wait for 100 ns;
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
report "Test failed for input combination: (169) 1010, 1001" severity
error;

s_b <= "1100"; s_a <= "1110"; wait for 100 ns;
assert ((s_B_greater_A = '0') and (s_B_equals_A = '0') and (s_B_less_A =
'1'))
report "Test failed for input combination: (206) 1100, 1110" severity
error;

s_b <= "1101"; s_a <= "0100"; wait for 100 ns;
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
report "Test failed for input combination: (212) 1101, 0100" severity
```

```


error;

s_b <= "1111"; s_a <= "1111"; wait for 100 ns;
assert ((s_B_greater_A = '1') and (s_B_equals_A = '0') and (s_B_less_A =
'0'))
report "Test failed for input combination: (255) 1111, 1111" severity
error;

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

end architecture testbench;

```

 

Console output with error at 255

```

[2021-02-23 16:27:42 EST] ghd1 -i design.vhd testbench.vhd && ghd1 -m tb_comparator_4bit && ghd1 -r tb_comparator_4bit --vcd=dump.vcd && sed -i 's/^U/X/g; s/^~/X/g; s/^H/1/g; s/^L/0/g' dump.vcd
analyze design.vhd
analyze testbench.vhd
elaborate tb_comparator_4bit
testbench.vhd:29:9:80ms:(report note): Stimulus process started
testbench.vhd:76:9:81200ns:(assertion error): Test failed for input combination: (255) 1111, 1111
testbench.vhd:79:9:81200ns:(report note): Stimulus process finished
Finding VCD file...
./dump.vcd
[2021-02-23 16:27:42 EST] Opening EPWave...
Done

```